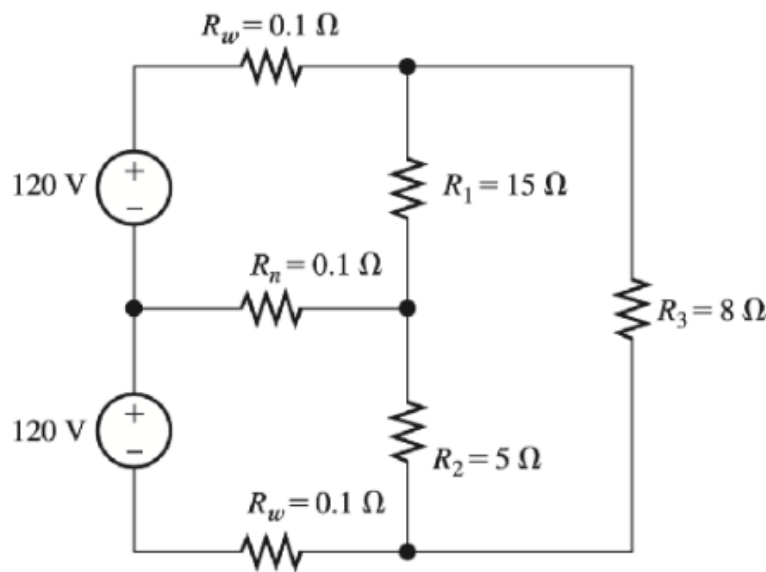


5. **(35 points)** The circuit shown in Figure 4.1 is the dc equivalent of a simple residential power distribution system. Each of the resistances labeled R_1 and R_2 represents various parallel-connected loads, such as lights or devices plugged into outlets that nominally operate at 120 V, while R_3 represents a load, such as the heating element in an oven that nominally operates at 240 V. The resistances labeled R_w represent the resistances of wires. R_n represents the “neutral” wire.
- a) Use mesh-current analysis to determine the voltage magnitude for R_n **(10pts)**. Write the equations in matrix form **(5pts)**. Use Matlab (or any other software) to solve the equations **(5 pts)**.
- b) Now suppose that due to a fault in the wiring at the distribution panel, the neutral wire becomes an open circuit. Again compute the voltages across the loads **(10pts)** and comment on the probable outcome for a sensitive device such as a computer or plasma television that is part of the 15Ω load **(5pts)**.



Circuit labeling (so our equations match)

- Top "hot" node on the right: A
- Middle node on the right (where the neutral wire connects): B
- Bottom "hot" node on the right: C

Components:

- Wire resistances $R_w = 0.1 \Omega$ on the top and bottom rails
- Neutral wire $R_n = 0.1 \Omega$
- Loads: $R_1 = 15 \Omega$ (between A and B), $R_2 = 5 \Omega$ (between B and C), $R_3 = 8 \Omega$ (between A and C)
- Two 120-V sources in series on the left (split-phase DC model), so top-left node is at 240 V, middle-left at 120 V, bottom-left at 0 V.

(a) Mesh analysis to get the neutral voltage V_n

Choose clockwise mesh currents

- i_1 : top-left rectangular loop (through top R_w , R_1 , R_n , and the upper 120-V source)
- i_2 : bottom-left rectangular loop (through bottom R_w , R_2 , R_n , and the lower 120-V source)
- i_3 : right rectangular loop (through R_1 , R_2 , R_3)

KVL for each mesh

(Shared elements appear with opposite signs; the source term is **+120** for both left meshes because, traversed clockwise, each source is crossed from $-$ to $+$.)

$$\begin{aligned} \text{(Top mesh)} \quad & (R_w + R_1 + R_n)i_1 - R_n i_2 - R_1 i_3 = +120 \\ \text{(Bottom mesh)} \quad & -R_n i_1 + (R_w + R_2 + R_n)i_2 - R_2 i_3 = +120 \\ \text{(Right mesh)} \quad & -R_1 i_1 - R_2 i_2 + (R_1 + R_2 + R_3)i_3 = 0 \end{aligned}$$

Matrix form

$$\underbrace{\begin{bmatrix} R_w + R_1 + R_n & -R_n & -R_1 \\ -R_n & R_w + R_2 + R_n & -R_2 \\ -R_1 & -R_2 & R_1 + R_2 + R_3 \end{bmatrix}}_{\mathbf{A}} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}}_{\mathbf{i}} = \underbrace{\begin{bmatrix} 120 \\ 120 \\ 0 \end{bmatrix}}_{\mathbf{b}}$$

Plugging $R_w = R_n = 0.1 \Omega$, $R_1 = 15 \Omega$, $R_2 = 5 \Omega$, $R_3 = 8 \Omega$ and solving $\mathbf{A}\mathbf{i} = \mathbf{b}$ gives

$$\boxed{i_1 = 36.75 \text{ A}}, \quad \boxed{i_2 = 51.56 \text{ A}}, \quad \boxed{i_3 = 28.89 \text{ A}}$$

These are the currents circulating in the three meshes; note that i_1 equals the current in the **top** R_w , i_2 equals the (left-to-right reference) current in the **bottom** R_w , and i_3 equals the current in R_3 .

Neutral voltage.

The current through the neutral resistor is the difference of the two left meshes across the shared R_n : $i_n = i_2 - i_1$.

Therefore

$$V_n = R_n(i_2 - i_1) = 0.1(51.56 - 36.75) = 1.48 \text{ V}$$

(magnitude). This matches the key.

Sanity check via node voltages (optional but reassuring):

$$V_A = 240 - i_1 R_w = 236.33 \text{ V}, \quad V_B = 120 - V_n = 118.52 \text{ V}, \quad V_C = i_2 R_w = 5.157 \text{ V}.$$

(b) Open neutral (fault): compute voltages across the loads

With R_n open, node B floats; R_1 and R_2 become a series string between A and C . Solve by nodal KCL at A, B, C :

$$\begin{aligned} \frac{V_A - 240}{R_w} + \frac{V_A - V_B}{R_1} + \frac{V_A - V_C}{R_3} &= 0 \\ \frac{V_B - V_A}{R_1} + \frac{V_B - V_C}{R_2} &= 0 \\ \frac{V_C - 0}{R_w} + \frac{V_C - V_B}{R_2} + \frac{V_C - V_A}{R_3} &= 0 \end{aligned}$$

Solving gives

$$V_A = 235.942 \text{ V}, \quad V_B = 62.029 \text{ V}, \quad V_C = 4.058 \text{ V}.$$

Hence the load voltages are

$$V_{R_3} = V_A - V_C = 231.884 \text{ V}, \quad V_{R_1} = V_A - V_B = 173.913 \text{ V}, \quad V_{R_2} = V_B - V_C = 57.971 \text{ V},$$

exactly as in the key.

What this means physically.

With the neutral open, the 120-V loads R_1 and R_2 no longer sit with respect to a stiff 120-V reference. They form a divider across the hot-to-hot potential, so the mid-node B "floats" to a value set by the ratio $R_1 : R_2 = 3 : 1$. That puts ~174 V across the 15-Ω branch and only ~58 V across the 5-Ω branch.

Power comparison (to see the danger):

$$P_{R_1} = \frac{V_{R_1}^2}{R_1} \approx \frac{(173.9)^2}{15} \approx 2.02 \text{ kW} \quad \text{vs.} \quad \frac{120^2}{15} = 0.96 \text{ kW (normal)}.$$

So the “120-V” devices on the $15 \, \Omega$ branch are severely **over-volted** (~45% high) and can fail catastrophically. The $5 \, \Omega$ branch is in brownout (~58 V), so devices there likely shut down or behave erratically. R_3 (the 240-V load) remains close to nominal voltage, aside from small drops in the hot conductors.